

## ERM 5500 – RF & Microwave Design

Department of Communications & Computer Engineering  
University of Malta

### Tutorial Sheet

1. For the receiver in Fig. 1, calculate:

- The noise figure of the system.
- The overall gain of the system.
- The minimum detectable signal at the input of the system.

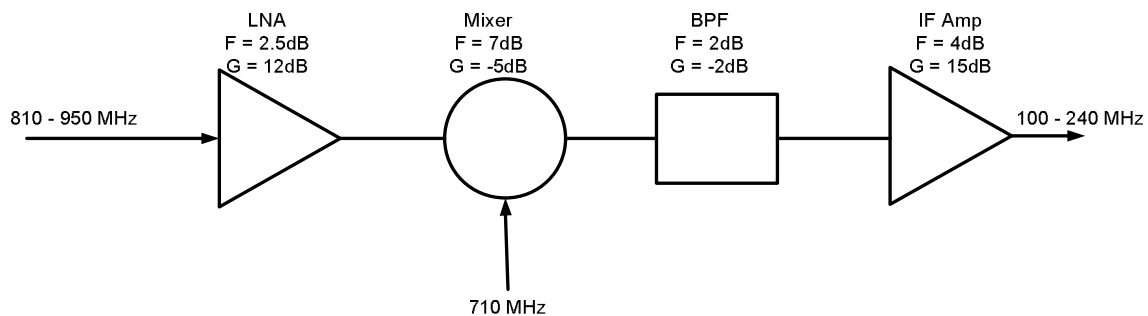


Figure 1

5. For the receiver in Fig. 2, calculate:

- The noise figure of the system.
- The overall gain of the system.
- The minimum detectable signal at the input of the system.

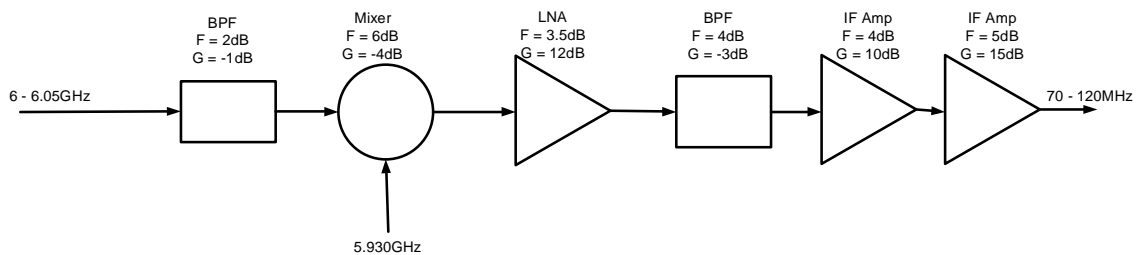


Figure 2

6. If the output power at the 1-dB compression point of an amplifier, having a gain of 12 dB over a bandwidth of 1.2 MHz and a noise figure of 2.5 dB, is 10 mW, calculate the dynamic range of the system.

7. The intercept point in the transfer characteristic of a nonlinear system is found to be 25 dBm. If a -5 dBm signal is applied to this system, find the intermodulation ratio.
8. A receiver operating at 900 MHz with its bandwidth at 1 MHz and noise figure at 16 dB. If its input impedance is  $50 \Omega$  and IP3 is 20 dBm, then find its dynamic range.
9. Discuss the following performance parameters:
  - (a) Minimum Detectible signal, (b) Gain compression, (c) Intermodulation Distortion Ratio, (d) Second-order harmonics, (e) Third-order intercept point, (f) Dynamic range
10. A nonlinear amplifier has transfer function  $v_{out} = 5v_{in} - 0.05v_{in}^2 - 0.1v_{in}^3$ , a noise figure of 3 dB and a bandwidth of 100 MHz. If an input signal  $v_{in} = 0.1\cos(1.01 \cdot 10^6 t) + 0.08\cos(1.012 \cdot 10^6 t)$  is applied to this circuit, calculate:
  - a. The noise of the system.
  - b. The gain compression.
  - c. The intermodulation distortion ratio.
  - d. The third-order intercept point.
  - e. The dynamic range.
11. A  $250 \Omega$  load is to be matched with a  $50 \Omega$  line. Design (a) a resistive network, and (b) a reactive network to match the load. Discuss the performance of the two designs.
12. Use the analytical approach to design a two-component matching network that matches a load  $Z_L = (80 + j20)\Omega$  to the source impedance  $Z_S = (10 + j25)\Omega$ , at a frequency of 1.2 GHz.
13. Design a two-component matching network for a load consisting of a  $40 \Omega$  resistor in series with a 2.5 nH inductor connected to a  $50 \Omega$  source. Determine the possible topologies that can be used and determine the component values at 500 MHz.
14. Design a T-type matching network that transforms  $Z_L = (100 - j25)\Omega$  to the source impedance  $Z_S = (20 - j40)\Omega$  at a nodal quality factor of  $Q = 4$ . Calculate the values at 900 MHz.

15. Design a Pi-type matching network that transforms  $Z_L = (100 - j25)\Omega$  to the source impedance  $Z_S = (20 - j40)\Omega$  at a nodal quality factor of  $Q = 4$ . Calculate the values at 900 MHz.
16. Analyze the heterodyne receiver architecture and compare it with the Image-reject receiver.
17. Design an active bias network for a BJT transistor operating at  $I_c = 12$  mA,  $V_{ce} = 2.5$  V and  $V_{cc} = 5$ V. Assume that both transistors have  $\beta = 150$  and  $V_{be} = 0.7$  V.
18. Determine the stability regions of a transistor whose measured S-parameters are:  $S_{11} = 0.6 \angle 45^\circ$ ,  $S_{12} = 0.2 \angle -20^\circ$ ,  $S_{21} = 6 \angle 75^\circ$ , and  $S_{22} = 0.5 \angle -45^\circ$ .
19. Given that a transistor is found to be unstable in the desired frequency range, indicate how this can be situation can be rectified to stabilize the circuit.